$0912_R16_COMP_III_CSC304_Sample_Questions$

| Q1. | Operating point represents |
|----------|---|
| Option A | Values of I _C and V _{CE} when signal is applied |
| Option B | The magnitude of signal |
| Option C | Zero signal values of I _C and V _{CE} |
| Option D | AC signal values |
| 1 | |
| Q2. | For proper amplification by a transistor circuit, the operating point should be |
| | located at the of the DC load line |
| Option A | The end point |
| Option B | Middle |
| Option C | The maximum current point |
| Option D | Below the cut-off |
| | |
| Q3. | In voltage divider bias, operating point is 3 V, 2 mA. If $V_{CC} = 9 \text{ V}$, $R_C = 2.2 \text{ k}\Omega$, |
| | what is the value of R _E ? |
| Option A | 2000Ω |
| Option B | 1400 Ω |
| Option C | 800Ω |
| Option D | 1600Ω |
| | |
| Q4. | In voltage divider bias, $V_{CC} = 25 \text{ V}$; $R_1 = 10 \text{ k}\Omega$; $R_2 = 2.2 \text{ V}$; $R_C = 3.6 \text{ V}$ and |
| | $R_E = 1 \text{ k}\Omega$. What is the emitter voltage? |
| Option A | 6.7 V |
| Option B | 5.3 V |
| Option C | 4.9 V |
| Option D | 3.8 V |
| | |
| Q5. | A silicon transistor is biased with base resistor method. If β =100, V_{BE} =0.7 V, zero |
| | signal collector current $I_C = 1$ mA and $V_{CC} = 6V$, what is the value of the base |
| | resistor R _B ? |
| Option A | 105 kΩ |
| Option B | 530 kΩ |
| Option C | 315 kΩ |
| Option D | 350 kΩ |
| | |
| Q6. | An LC oscillator cannot be used to produce frequencies |
| Option A | High |
| Option B | Audio |
| Option C | Very low |
| Option D | Very high |
| | |
| Q7. | The piezoelectric effect in a crystal is |

| Option A | A voltage developed because of mechanical stress |
|----------|---|
| Option B | A change in resistance because of temperature |
| Option C | A change in frequency because of temperature |
| Option D | A voltage developed because of electrical signal |
| - F | - S |
| Q8. | The crystal oscillator frequency is very stable due to of the crystal |
| Option A | Rigidity |
| Option B | Vibrations |
| Option C | Low Q |
| Option D | High Q |
| | |
| Q9. | A second condition of Barkhausen criteria for oscillations is |
| Option A | A gain of 1 around the feedback loop |
| Option B | No gain around the feedback loop |
| Option C | The attention of the feedback circuit must be one-third |
| Option D | The feedback circuit must be capacitive |
| | • |
| Q10. | Which of the following amplifier class have highest linearity and lowest |
| | distortion? |
| Option A | Class A |
| Option B | Class B |
| Option C | Class C |
| Option D | Class AB |
| | |
| Q11. | Which type of power amplifier is biased for operation at greater than 180° of the |
| | cycle? |
| Option A | Class A |
| Option B | Class B |
| Option C | Class C |
| Option D | Class AB |
| | |
| Q12. | The ability of the receiver to select the wanted signals among the various |
| | incoming signals is termed as |
| Option A | Sensitivity |
| Option B | Selectivity |
| Option C | Stability |
| Option D | Fidelity |
| | |
| Q13. | Standard intermediate frequency used for AM receiver is |
| Option A | 455 MHz |
| Option B | 455 kHz |
| Option C | 455 Hz |
| Option D | 45.5 kHz |
| | |

| Q14. | Calculate the bandwidth occupied by a DSB signal when the modulating |
|----------|--|
| | frequency lies in the range from 100 Hz to 10KHz. |
| Option A | 28 KHz |
| Option B | 24.5 KHz |
| Option C | 38.6 KHz |
| Option D | 19.8 KHz |
| 015 | The function of multipleving is |
| Q15. | The function of multiplexing is To reduce the bandwidth of the signal to be transmitted |
| Option A | |
| Option B | To combine multiple data streams over a single data channel |
| Option C | To allow multiple data streams over multiple channels in a prescribed format |
| Option D | To match the frequencies of the signal at the transmitter as well as the receiver |
| Q16. | AM wave may be represented as $E(t) \cos \omega_c t$ where $E(t)$ is |
| Option A | Envelope of the AM wave |
| Option B | Carrier signal |
| Option C | Amplitude of modulating signal |
| Option D | Modulating signal |
| 1 | |
| Q17. | Advantage of using direct method for generation of FM signal is |
| Option A | It gives high stability to FM signal frequency |
| Option B | Distortion free FM signal is generated |
| Option C | High power FM generation is possible |
| Option D | Low power FM generation is possible |
| • | • |
| Q18. | The digital modulation technique in which the step size is varied according to the |
| | variation in the slope of the input is called |
| Option A | Delta modulation |
| Option B | PCM |
| Option C | Adaptive delta modulation |
| Option D | PAM |
| 0.10 | |
| Q19. | The information rate R for given average information H= 2.0 for analog signal |
| | band limited to B Hz is |
| Option A | 8 B bits/sec |
| Option B | 4 B bits/sec |
| Option C | 2 B bits/sec |
| Option D | 16 B bits/sec |
| 0.20 | |
| Q20. | The information I contained in a message with probability of occurrence is given |
| | by (k is constant). |
| Option A | $I = k \log_2 1/P$ |
| Option B | $I = k \log_2 P$ |
| Option C | $I = k \log_2 1/2P$ |
| Option D | $I = k \log_2 1/P^2$ |

| Q21. | The Op-amp can amplify |
|----------|---|
| Option A | a.c. signals only |
| Option B | a.c. signals only |
| Option C | both a.c. and d.c. signals |
| Option D | neither d.c. nor a.c. signals |
| | |
| Q22. | The input stage of an Op-amp is usually a |
| Option A | differential amplifier |
| Option B | class B push-pull amplifier |
| Option C | CE amplifier |
| Option D | swamped amplifier |
| | |
| Q23. | For an Op-amp with negative feedback, the output is |
| Option A | equal to the input |
| Option B | increased |
| Option C | fed back to the inverting input |
| Option D | fed back to the noninverting input |
| | |
| Q24. | In PCM, the parameter varied in accordance with the amplitude of the modulating |
| | signal is |
| Option A | Amplitude |
| Option B | Frequency |
| Option C | Phase |
| Option D | Code |
| | |
| Q25. | Granular noise occurs when |
| Option A | Step size is too small |
| Option B | Step size is too large |
| Option C | There is interference from the adjacent channel |
| Option D | Bandwidth is too large |